

Department of Software Engineering

Lab 2

Course:	CALD	Instructor:	Engr. Sidra Rafique
Topic:	Verification of Basic Logic Gates & their Truth tables		Deadline: 22-4-2025

Objective: To study and understand the basic functioning and truth tables of various logic gates including AND, OR, NOT, NAND, NOR, and XOR.

APPARATUS: Power Supply, Breadboard, Connecting wires.(virtually)

THEORY: Logic gates are the digital circuits with one output and one or more inputs. They are the basic building blocks of any logic circuit. Different logic gates are: AND, OR, NOT, NAND, NOR, XOR. They work according to certain logic.

1. AND: Logic equation. $Y = A.B$

The output of AND gate is logic 1 when both the inputs A and B are at high logic.

2. OR: Logic eqn. $Y = A+B$.

The output of OR gate is logic 1 when either one of the inputs A or B or both the inputs are logic 1.

3. NOT: Logic eqn. $Y = \bar{A}$.

The output of NOT gate is complement of the input.

4. NAND: Logic eqn. $Y = \sim(A.B)$ or $Y = (A.B)'$

The output of NAND gate is high logic or logic 1 when one of the inputs or both the inputs are low level.

5. NOR: Logical eqn. $Y = A+B$.

The output of NOR gate is true when both the inputs are low.


6. X-OR: Logic eqn. $Y = AB + \bar{A}\bar{B}$.

The output of XOR gate is true when both inputs are complemented of each other.

IC PINOUTS

TRUTH-TABLE


7400

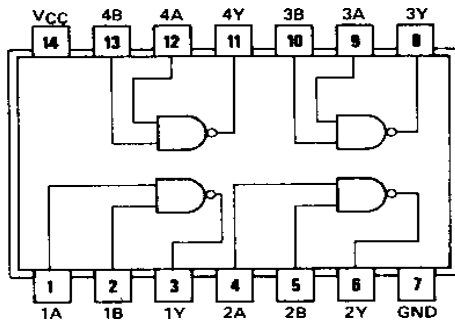

NAND-7400

A	B	Y
0	0	
0	1	
1	0	
1	1	


7402

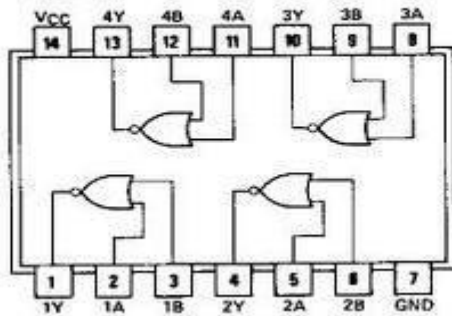

NOR-7402

A	B	Y
0	0	
0	1	
1	0	
1	1	


7404

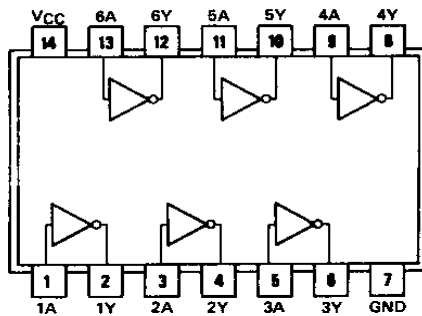

NOT- 7404

A	Y
0	
1	


7408

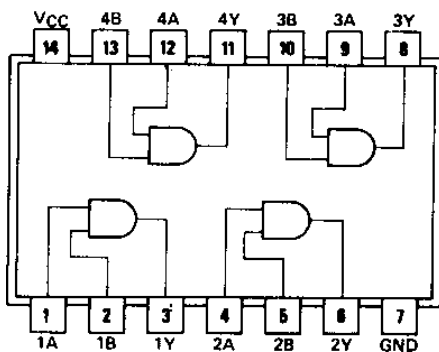

AND- 7408

A	B	Y
0	0	
0	1	
1	0	
1	1	


7432

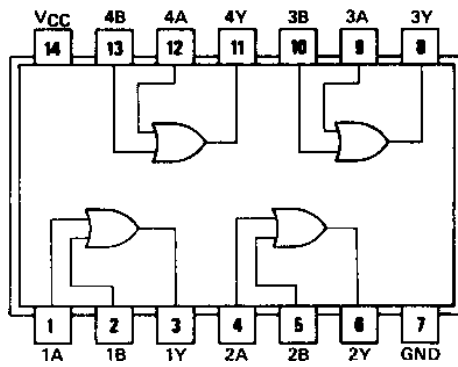

OR- 7432

A	B	Y
0	0	
0	1	
1	0	
1	1	

7486

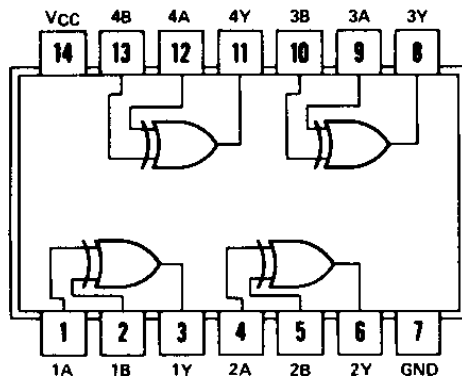

XOR- 7486

A	B	Y
0	0	
0	1	
1	0	
1	1	

Procedure:

Write procedure to make connections using EWB in your Own words.