

THE UNIVERSITY OF AZAD JAMMU & KASHMIR, MUZAFFARABAD



COURSE TITLE	CALD
COURSE CODE	CS-1205
LAB TITLE	HALF ADDER
STUDENT NAME	HASEEB SHEIKH
STUDENT ROLL NUMBER	2024-SE-31
INSTRUCTOR NAME	ENGR. SIDRA RAFIQUE
SUBMISSION DATE	JUNE 04, 2025

DEPARTMENT OF SOFTWARE ENGINEERING

# CALD

## Lab 4

### Objective:

This experiment aims to demonstrate the working of the half adder.


## Experiment on EWB

### 1: Verification using a probe

#### First Combination:

- Switch Q: 1
- Switch W: 0


+ve power supply

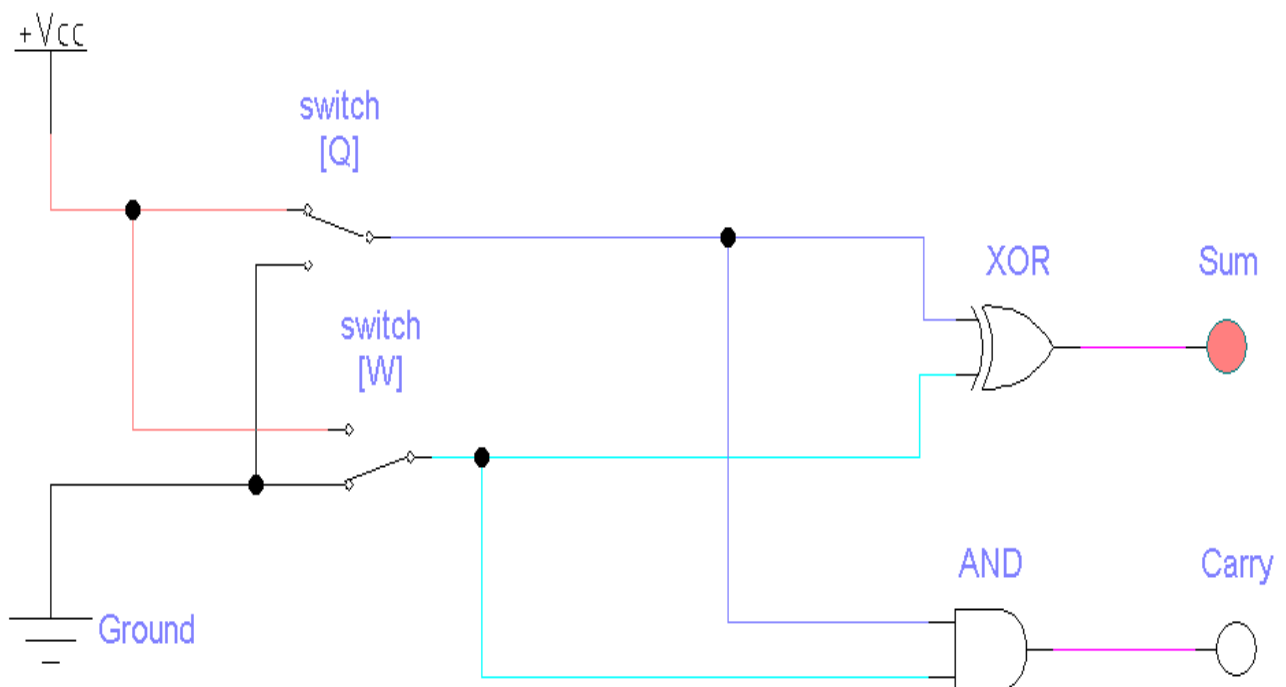

## Second Combination:

- Switch Q: 0
- Switch W: 1


+ve power supply

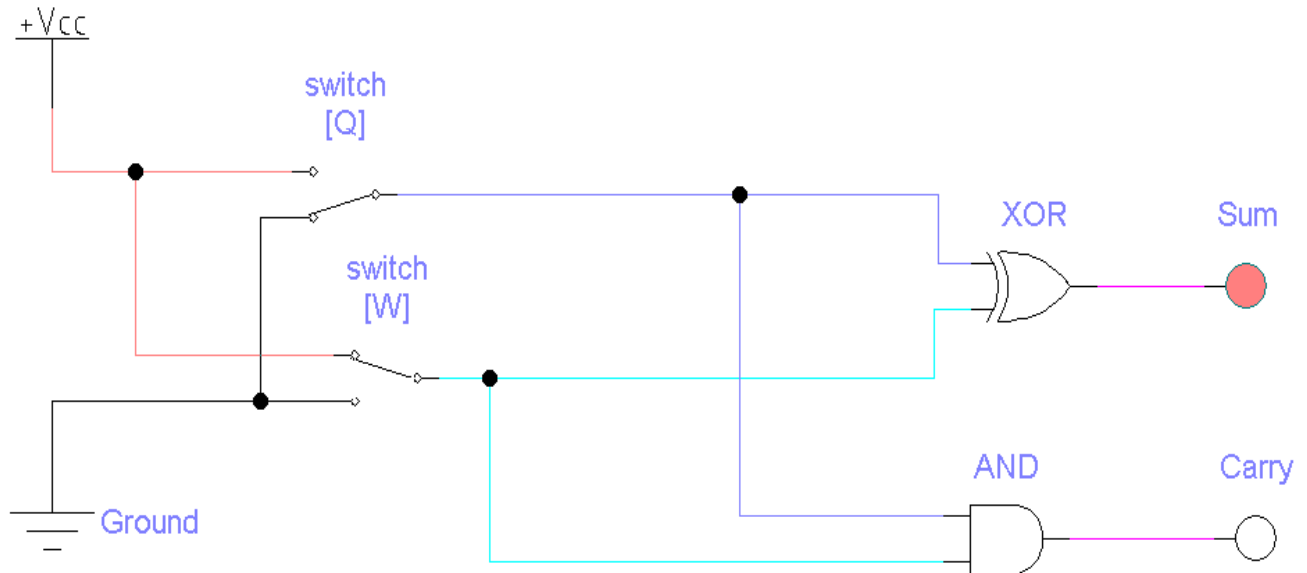

## Third Combination:

- Switch Q: 1
- Switch W: 1


+ve power supply

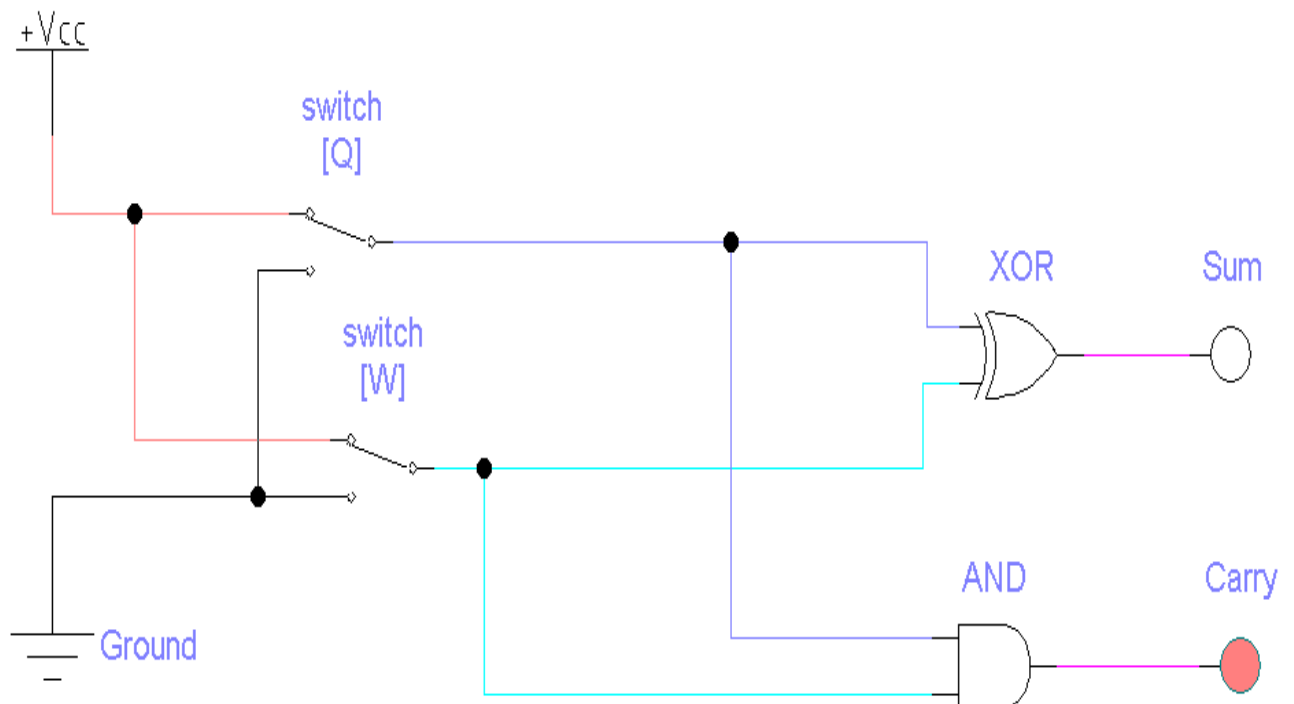

## 2: Verification using ICs


### First Combination:

- Switch Q; 1
- Switch W: 0

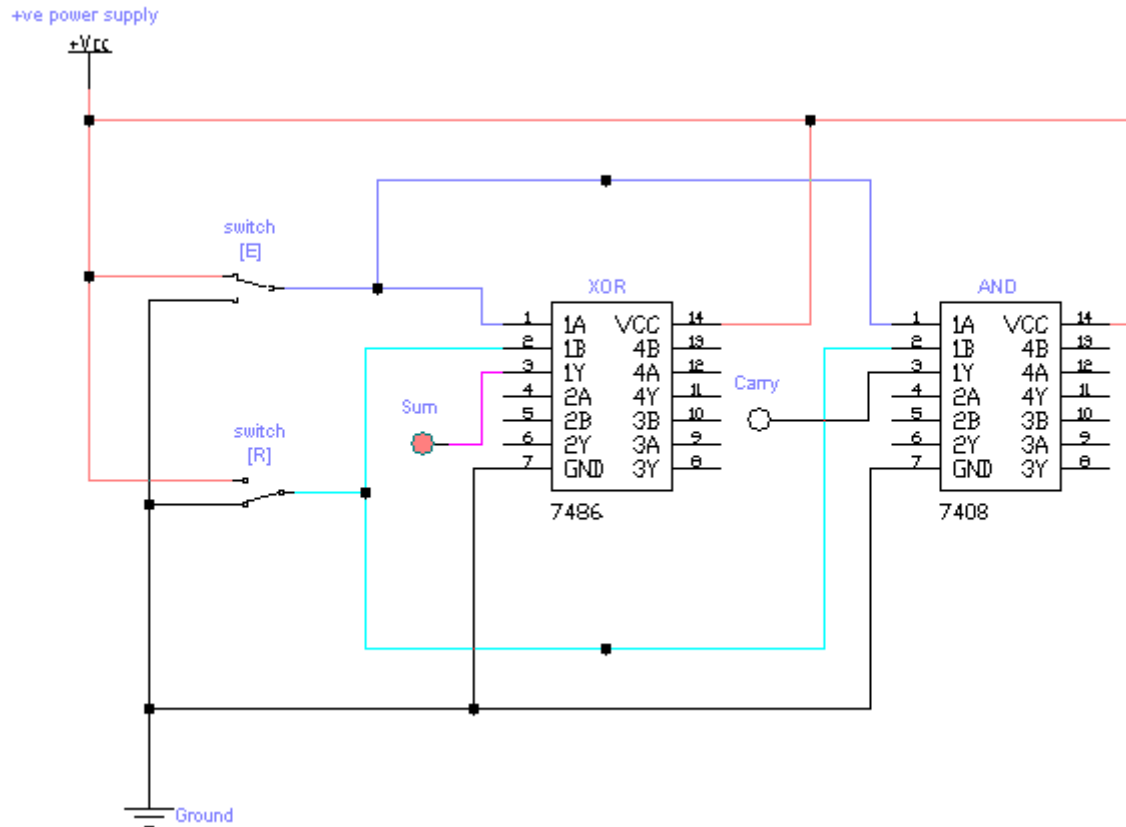


### Second Combination:

- Switch Q: 0
- Switch W: 1

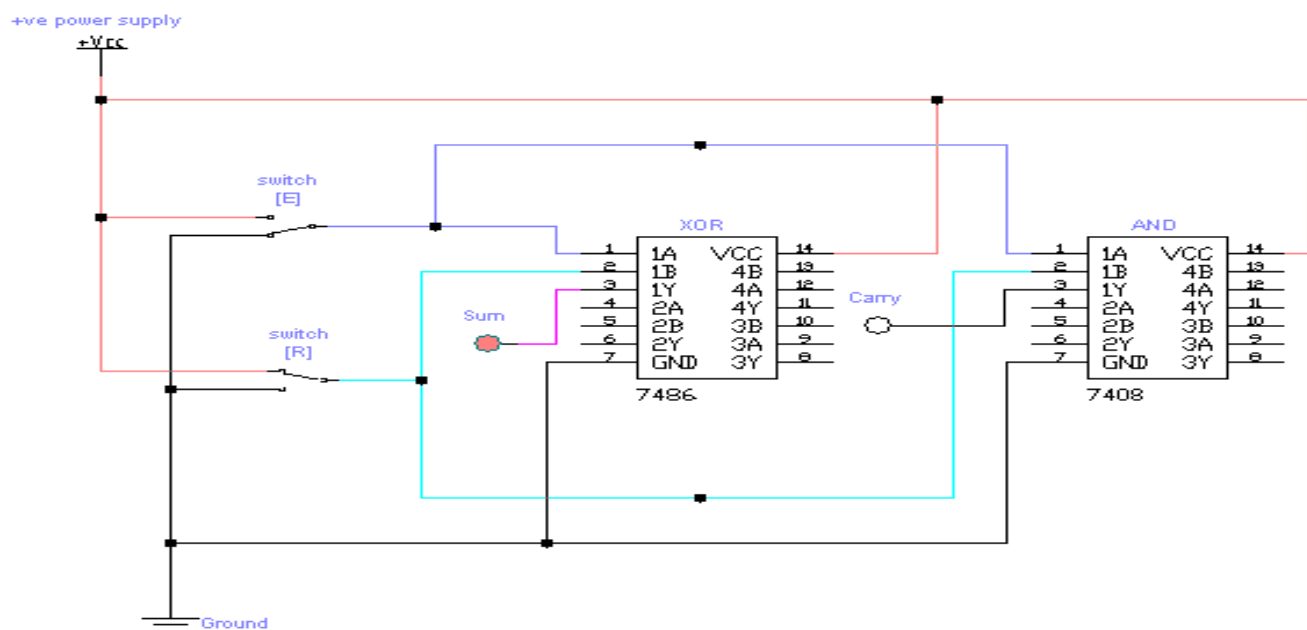

### Third Combination:


- Switch Q: 1
- Switch W: 1

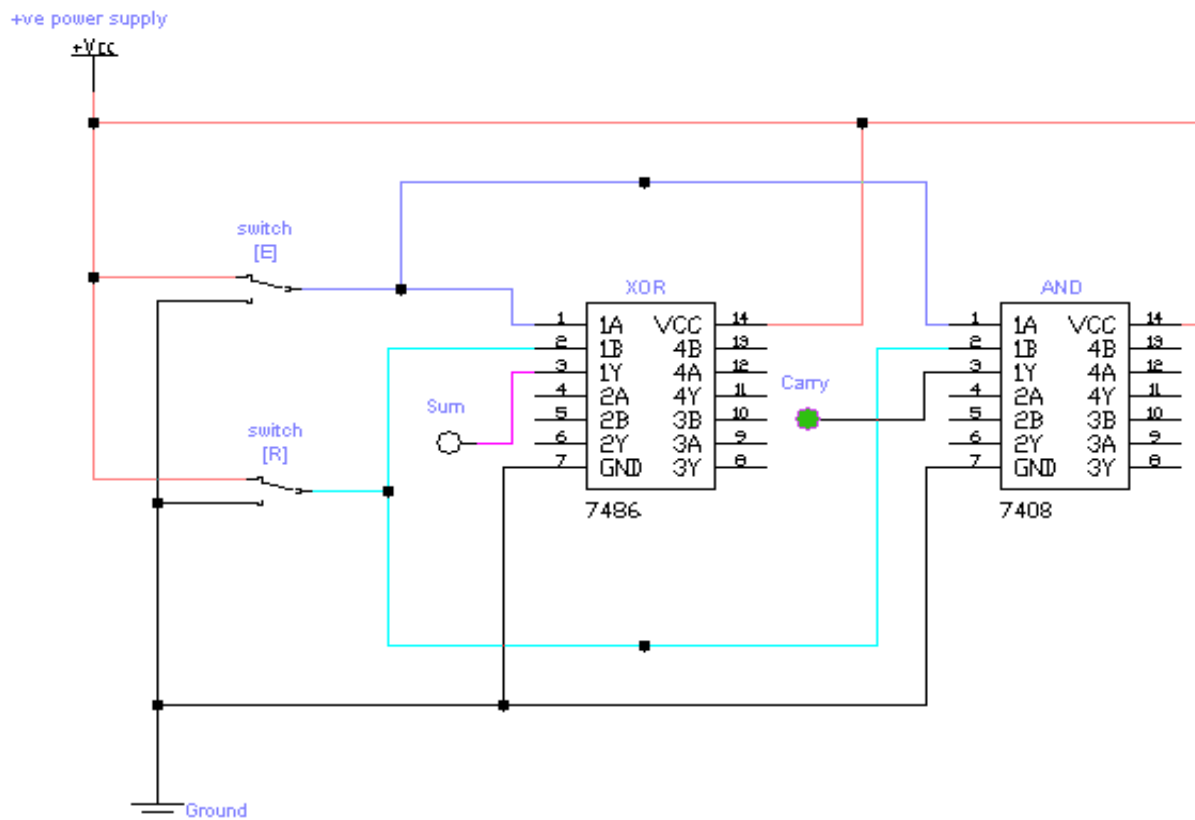

## 3: Complicated Circuit


### First Combination:

- Switch Q; 1
- Switch W: 0

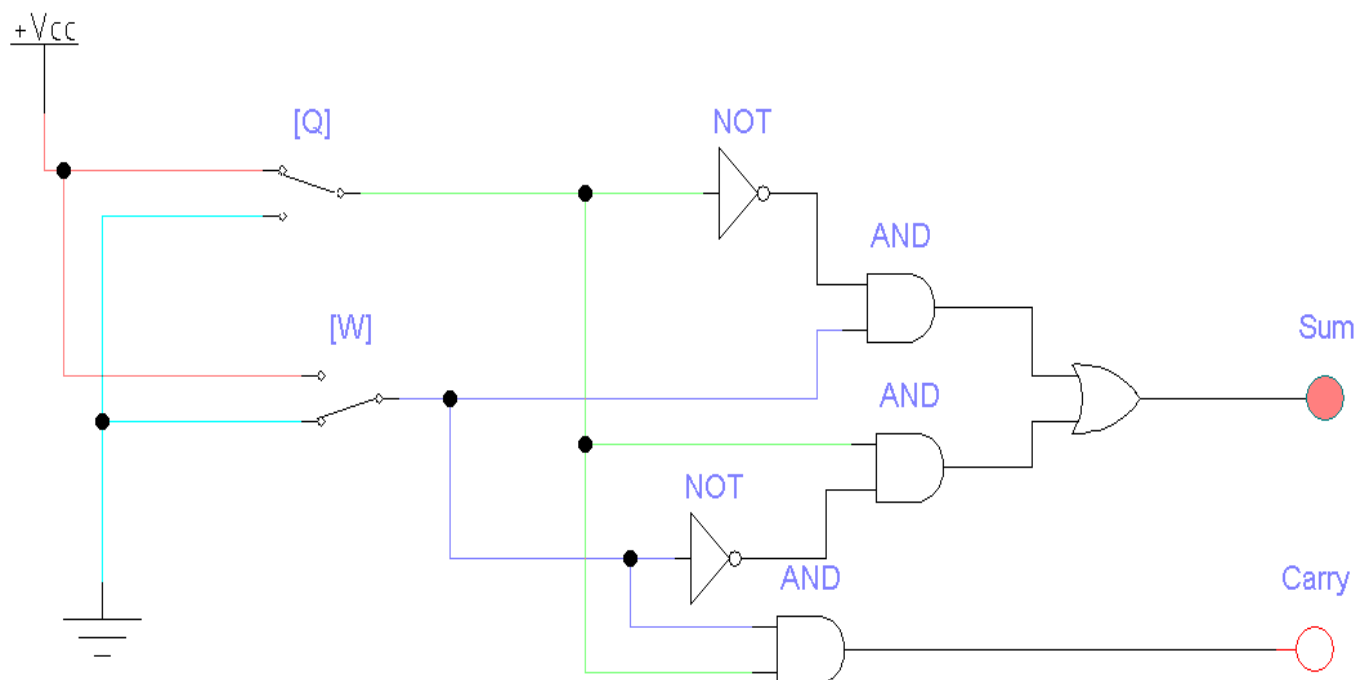


## Second Combination:

- Switch Q; 0
- Switch W: 1

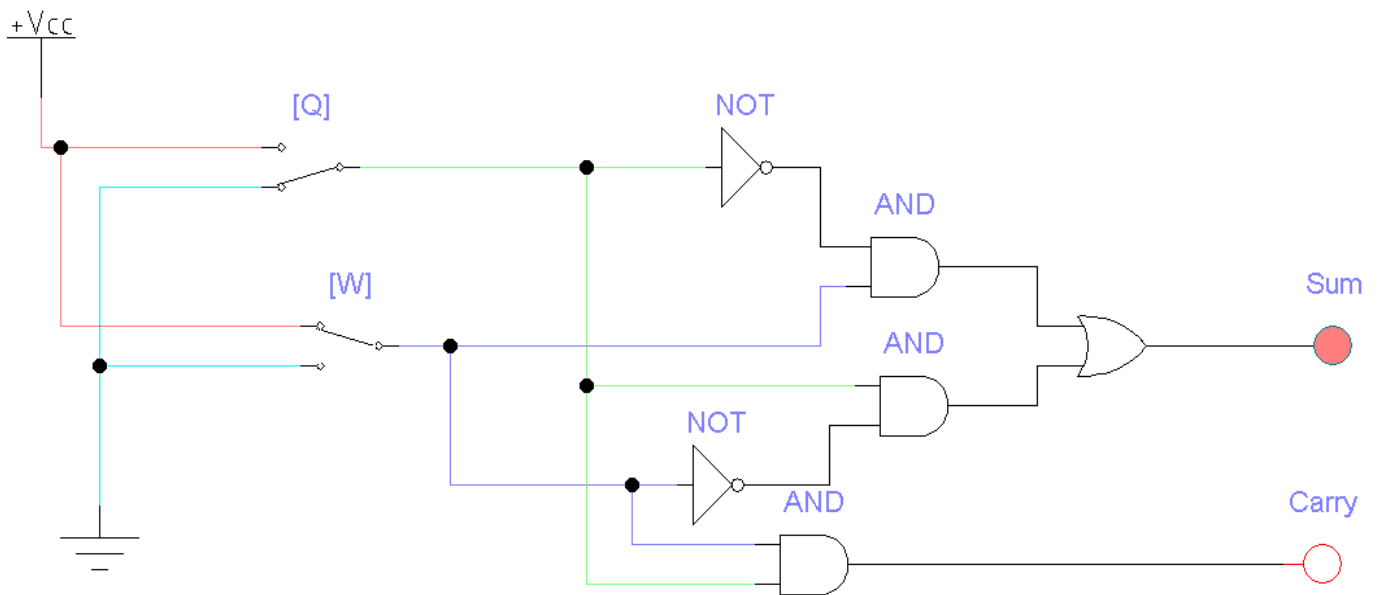


## Third Combination:

- Switch Q; 1
- Switch W: 1

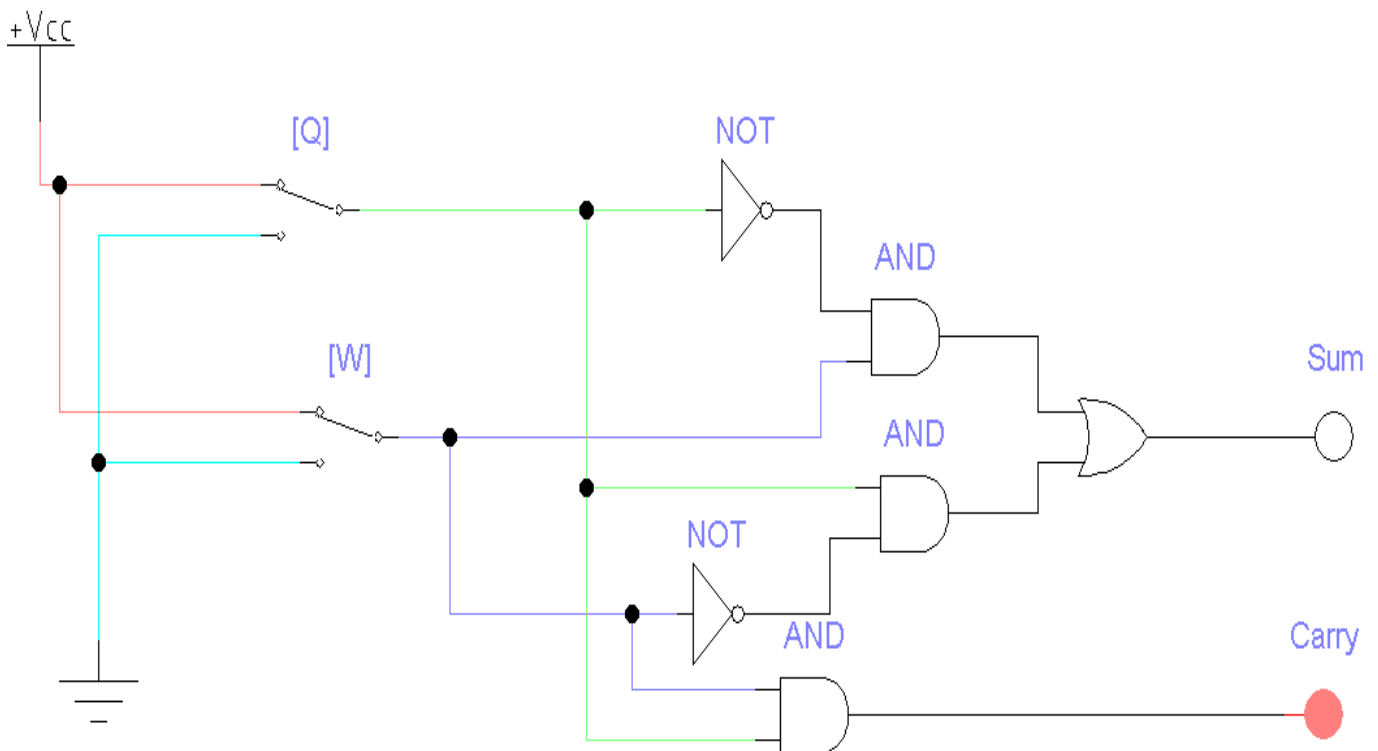

# Experiment on Hardware

## 4: Simple Circuit Implementation

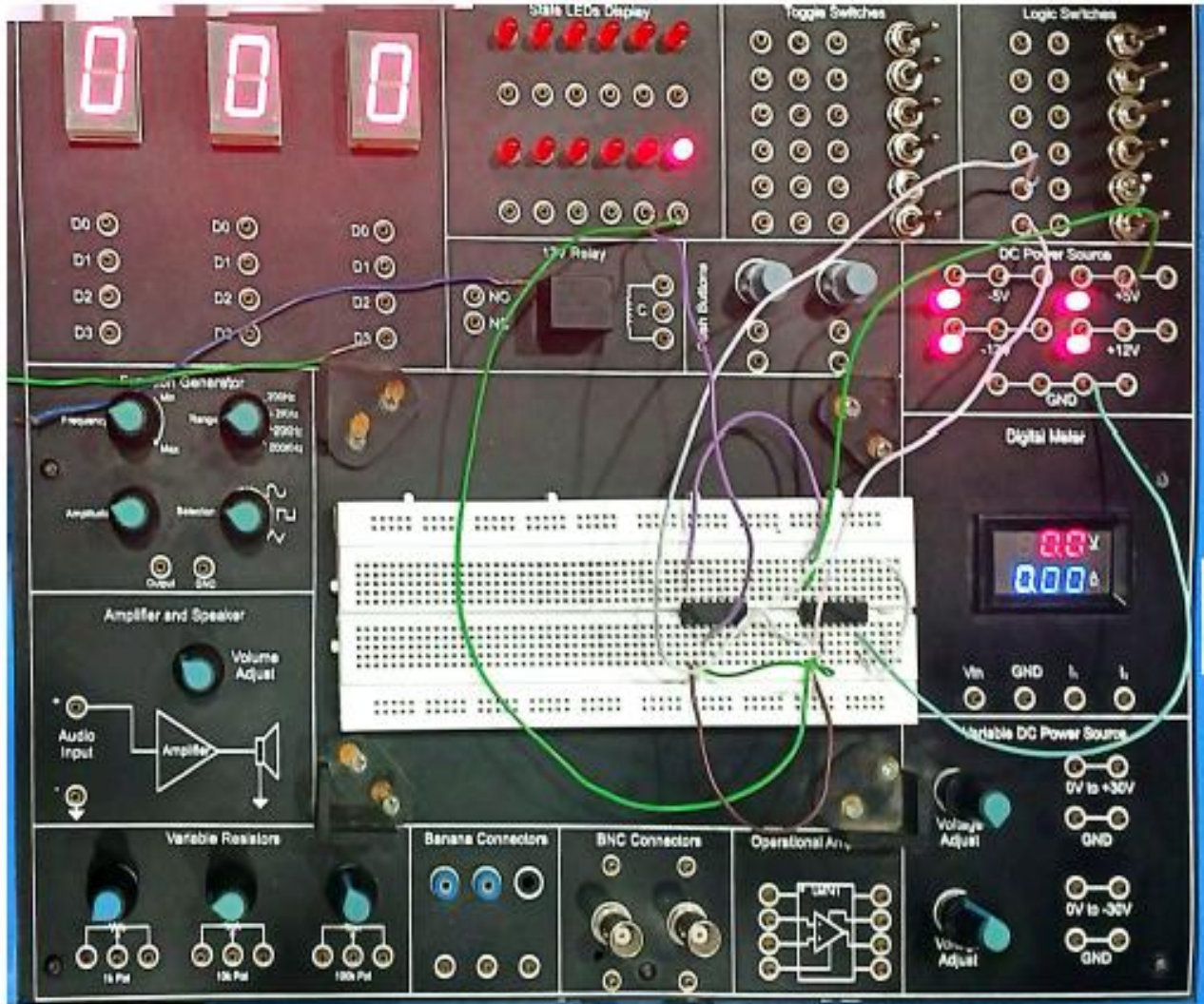

- Circuit shows the implementation of Half Adder using ICs of XOR and AND.



## 5: Complicated Circuit Implementation

